

Chapter 6 Microwave Resonators

Part I

1. Series and Parallel Resonant Circuits
2. Loss and Q Factor of a Resonant Circuit
3. Various Waveguide Resonators
4. Coupling to a Lossy Resonator

Part II

- Time-Domain Analysis of Open Cavities


Part III

- Spectral-Domain Analysis of Open Cavities

1

6.1 Series and Parallel Resonant Circuits

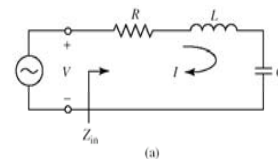(1) Series Resonant Circuit $Z_{in} = R + j\omega L + (j\omega C)^{-1}$




$$P_{in} = \frac{1}{2} VI^* = \frac{1}{2} |I|^2 Z_{in} = P_{loss} + 2j\omega(W_m - W_e) \Rightarrow Z_{in} = \frac{2P_{in}}{|I|^2}$$

$$\text{Power dissipation : } P_{loss} = \frac{1}{2} |I|^2 R$$

$$\text{Energy stored in } L : W_m = \frac{1}{4} |I|^2 L$$

$$\text{Energy stored in } C : W_e = \frac{|I|^2}{4\omega^2 C}$$

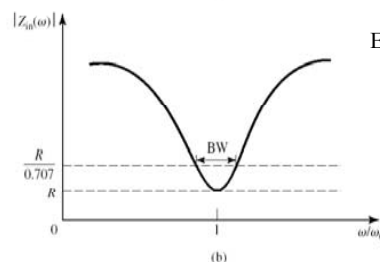

- Resonance occurs at $W_m = W_e$, $Z_{in} = R$, and $\omega = \omega_0 = 1/\sqrt{LC}$.

- Quality factor :

$$Q \equiv \omega \frac{\text{Average energy stored}}{\text{Energy loss per second}} = \omega_0 \frac{2W_m}{P_{loss}} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

2

Series Resonant Circuit

Near Resonance $\omega = \omega_0 + \Delta\omega$, $\Delta\omega$ is small.


$$\begin{aligned} Z_{in} &= R + j\omega L \left(1 - \frac{1}{\omega^2 LC}\right) \\ &= R + j\omega L \left(\frac{\omega^2 - \omega_0^2}{\omega^2}\right) \\ &\approx R + j2\Delta\omega L = R + j2\frac{QR}{\omega_0} \Delta\omega, \quad Q \equiv \frac{\omega_0 L}{R} \end{aligned}$$

Complex frequency: $\omega \leftarrow \omega_0 \left(1 + \frac{j}{2Q}\right)$

- If $R=0$ or lossless case,


$$\begin{aligned} Z_{in} &\approx j2L\Delta\omega = j2L(\omega - \omega_0) \\ &\rightarrow j2L \left[\omega - \omega_0 \left(1 + \frac{j}{2Q}\right) \right] = j2L(\omega - \omega_0) + \frac{\omega_0 L}{Q} \\ &= j2L(\omega - \omega_0) + R \end{aligned}$$

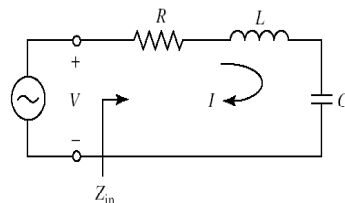- A resonator with loss can be treated as a *lossless resonator* whose resonant frequency ω_0 is replaced by a complex frequency $\omega_0(1 + j/2Q)$



3

Parallel Resonant Circuit

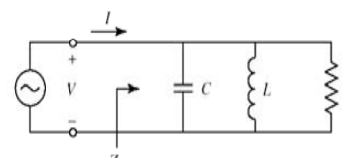


$$Z_{in} = \left[\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right]^{-1}$$

$$\text{Power dissipation : } P_{loss} = \frac{1}{2} \frac{|V|^2}{R}$$

$$\text{Energy stored in } C : W_e = \frac{1}{4} C |V|^2$$

$$\text{Energy stored in } L : W_m = \frac{1}{4} \frac{|V|^2}{\omega^2 L}$$

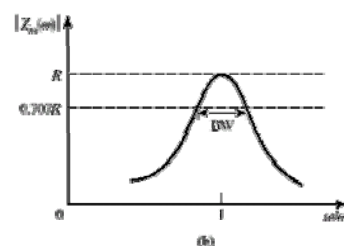


- Complex power delivered to the resonator

$$\begin{aligned} P_{in} &= \frac{1}{2} VI^* = \frac{1}{2} \frac{|V|^2}{Z_{in}^*} = \frac{1}{2} |V|^2 \left(\frac{1}{R} - \frac{1}{j\omega L} - j\omega C \right) \\ &= P_{loss} + 2j\omega(W_m - W_e) \end{aligned}$$

- Input impedance at resonance, $Z_{in} = R$, $W_m = W_e$, $\omega_0 = \frac{1}{\sqrt{LC}}$

4

Parallel Resonant Circuit

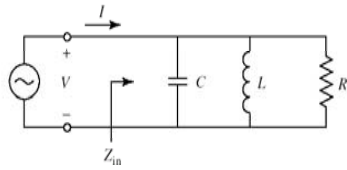

$$Q \equiv \omega \frac{\text{Average energy stored}}{\text{Energy loss per second}}$$

$$= \omega_0 \frac{2W_m}{P_{\text{loss}}} = \frac{R}{\omega_0 L} = \omega_0 RC$$


$$Z_{in} = \left[\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right]^{-1}, \text{ near resonance } \omega = \omega_0 + \Delta\omega$$

$$\approx \left[\frac{1}{R} + \frac{1 - \frac{\Delta\omega}{\omega_0}}{j\omega_0 L} + j(\omega_0 + \Delta\omega)C \right]^{-1} = \left(\frac{1}{R} + j2\Delta\omega C \right)^{-1}$$

$$= \frac{R}{1 + j2\Delta\omega RC} = \frac{R}{1 + j2Q \frac{\Delta\omega}{\omega_0}} \xrightarrow{R \rightarrow \infty} \frac{1}{j2(\Delta\omega)C}$$

5

Parallel Resonant Circuit

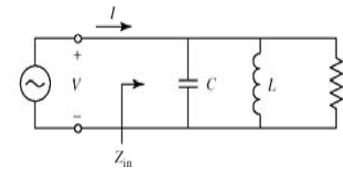

The loss factor can be accounted by using $\omega_0 \leftarrow \omega_0 (1 + j/2Q)$.

$$Q = \omega_0 \frac{2W_m}{P_{\text{loss}}} = \frac{R}{\omega_0 L} = \omega_0 RC$$

$$\text{Fractional bandwidth} = 2\Delta\omega/\omega_0 = Q^{-1}$$

$$|Z_{in}(\omega)| = \frac{R}{\sqrt{2}}$$

$$\frac{1}{j\omega C + (j\omega L)^{-1}} = \frac{j\omega L}{1 - \omega^2 LC} = \pm jR$$

$$\omega^2 LC - 1 = \pm \frac{\omega L}{R},$$

$$\left(\frac{\omega}{\omega_0} \right)^2 \pm \frac{1}{Q} \left(\frac{\omega}{\omega_0} \right) - 1 = 0 \leftarrow \text{Quadratic equation}$$

$$\text{if } R \rightarrow \infty, Z_{in} \approx \frac{1}{j2(\Delta\omega)C}$$

$$2(\Delta\omega)C = j2C(\omega - \omega_0)$$

$$\omega_0 \leftarrow \omega_0 (1 + j/2Q)$$

$$j2C \left[\omega - \omega_0 \left(1 + \frac{j}{2Q} \right) \right]$$

$$= j2C(\omega - \omega_0) + \frac{\omega_0 C}{Q} = j2C\Delta\omega + \frac{1}{R}$$

$$\frac{\omega}{\omega_0} = \frac{1}{2} \left(\mp \frac{1}{Q} + \sqrt{\frac{1}{Q^2} + 4} \right) \Rightarrow \frac{\omega_1 - \omega_2}{\omega_0} = \frac{1}{Q}$$


6

Loaded and Unloaded Q

- Unloaded Q (Load resistance $R_L \rightarrow \infty$)

$$\text{Series Resonance: } Q = (\omega_0 RC)^{-1} = \omega_0 L/R$$
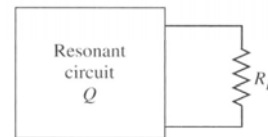
$$\text{Parallel Resonance: } Q = \omega_0 RC = R/\omega_0 L$$



- External Q, $Q_e = \begin{cases} \frac{\omega_0 L}{R_L}, & \text{for series resonant circuits;} \\ \frac{R_L}{\omega_0 L}, & \text{for parallel resonant circuits.} \end{cases}$

- Loaded Q, or Q_L , of a resonant circuit with a load of R_L


$$\text{Series Resonance: } Q_L = \frac{\omega_0 L}{R + R_L} \Rightarrow \frac{1}{Q_L} = \frac{1}{Q_e} + \frac{1}{Q}$$

$$\text{Parallel Resonance: } Q_L = \frac{R // R_L}{\omega_0 L} \Rightarrow \frac{1}{Q_L} = \frac{1}{Q_e} + \frac{1}{Q}, \quad \frac{1}{R // R_L} = \frac{1}{R} + \frac{1}{R_L}$$

7

Summary

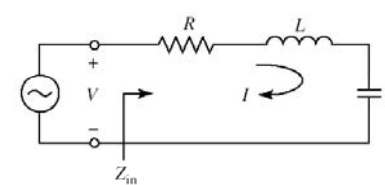- (1) Model for a Series Resonant Circuit




$$Q \equiv \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

$$Z_{in} \approx R + j2L\Delta\omega = R + j2(\omega - \omega_0)L$$

- A lossless series resonant circuit is short-circuited at ω_0 and has $Q \rightarrow \infty$

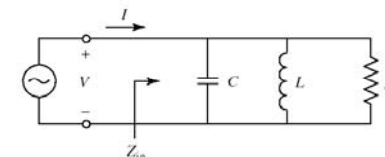- (2) Model for a Parallel Resonant Circuit



$$Q \equiv \frac{R}{\omega_0 L} = \omega_0 RC$$

$$Y_{in} \approx \frac{1}{R} + j2C\Delta\omega = \frac{1}{R} + j2C(\omega - \omega_0)$$


- A lossless parallel resonant circuit is short-circuited at ω_0 and has $Q \rightarrow \infty$

8

6.2 Transmission Line Resonators

- All realistic resonators have a finite $Q=f_0/BW$
 - ⇒ Nonzero bandwidth ⇒ Resonator is lossy
 - ⇒ Transmission line resonator has an $\alpha \neq 0$
 - ⇒ Lossy transmission line

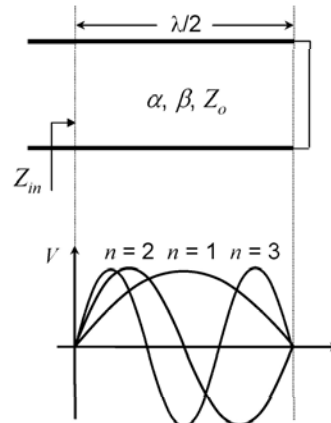- (1) Short circuit $\lambda/2$ line ⇒ series resonance
- If loss is small, $\alpha\ell \ll 1$, $\tan \alpha\ell \approx \alpha\ell$.
 - Near resonance, $\omega = \omega_0 + \Delta\omega$, $\Delta\omega$ is small.
 - What is the equivalent circuit?




9

6.2 Transmission Line Resonators

- (1) Short-circuit $\lambda/2$ line section

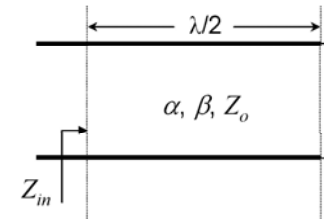(a) $\tanh \alpha\ell \approx \alpha\ell$, (b) $\Delta\omega$ is small.




$$\beta\ell = \frac{\omega_0\ell + \Delta\omega\ell}{v_p} = \pi \left(1 + \frac{\Delta\omega}{\omega_0} \right) \Rightarrow \tan \beta\ell \approx \frac{\Delta\omega}{\omega_0} \pi$$

$$Z_{in} = Z_0 \tanh(\alpha + j\beta)\ell = Z_0 \frac{\tanh \alpha\ell + j \tan \beta\ell}{1 + j \tanh \alpha\ell \tan \beta\ell}$$

$$\approx Z_0 \frac{\alpha\ell + j \frac{\Delta\omega}{\omega_0} \pi}{1 + j \alpha\ell \frac{\Delta\omega}{\omega_0} \pi} \approx Z_0 \left(\alpha\ell + j \frac{\Delta\omega}{\omega_0} \pi \right)$$

$$\rightarrow R + 2jL\Delta\omega$$

Equivalent circuit :

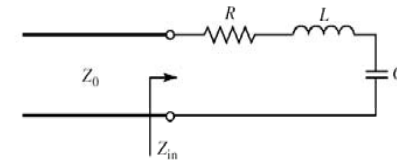

$$R = Z_0\alpha\ell, L = \frac{\pi Z_0}{2\omega_0}, C = \frac{1}{\omega_0^2 L}$$

$$Q = \frac{\omega_0 L}{R} = \frac{\pi}{2\alpha\ell} = \frac{\beta}{2\alpha}$$

10

Transmission Line Resonators

- (2) Short-circuit $\lambda/4$ line ⇒ parallel resonance
- If loss is small, $\alpha\ell \ll 1$, $\tan \alpha\ell \approx \alpha\ell$.
 - Near resonance, $\omega = \omega_0 + \Delta\omega$, $\Delta\omega$ is small.


$$Z_{in} = Z_0 \tanh(\alpha + j\beta)\ell = Z_0 \frac{1 - j \tanh \alpha\ell \cot \beta\ell}{\tanh \alpha\ell - j \cot \beta\ell}$$

$$\beta\ell = \frac{\pi}{2} \left(1 + \frac{\Delta\omega}{\omega_0} \right), \cot \beta\ell = -\tan \left(\frac{\pi}{2} \frac{\Delta\omega}{\omega_0} \right) \approx -\frac{\pi}{2} \frac{\Delta\omega}{\omega_0}$$


$$Z_{in} \approx \frac{Z_0}{\alpha\ell + j \frac{\pi}{2} \frac{\Delta\omega}{\omega_0}} \equiv \frac{1}{\frac{1}{R} + 2j\Delta\omega C}$$

$$C = \frac{\pi}{4\omega_0 Z_0}, R = \frac{Z_0}{\alpha\ell}, L = \frac{1}{\omega_0^2 C}$$
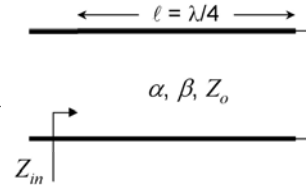
$$Q = \omega_0 RC = \frac{\pi}{4\alpha\ell} = \frac{\beta}{2\alpha}, \ell = \frac{\pi}{2\beta} \text{ at resonance.}$$



Equivalent circuit :

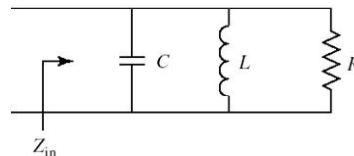

11

Transmission Line Resonators

- (3) Open-circuit $\lambda/2$ line ⇒ parallel resonance

- If loss is small, $\alpha\ell \ll 1$, $\tan \alpha\ell \approx \alpha\ell$.
- Near resonance, $\omega = \omega_0 + \Delta\omega$, $\Delta\omega$ is small.


$$Z_{in} = Z_0 \coth(\alpha + j\beta)\ell = Z_0 \frac{1 + j \tanh \alpha\ell \tan \beta\ell}{\tanh \alpha\ell + j \tan \beta\ell}$$

$$\beta\ell = \pi \times \left(1 + \frac{\Delta\omega}{\omega_0} \right), \tan \beta\ell = \tan \left(\pi \frac{\Delta\omega}{\omega_0} \right) \approx \pi \frac{\Delta\omega}{\omega_0}$$


$$Z_{in} \approx \frac{Z_0}{\alpha\ell + j \pi \frac{\Delta\omega}{\omega_0}} \equiv \frac{1}{\frac{1}{R} + 2j\Delta\omega C}$$

$$C = \frac{\pi}{2\omega_0 Z_0}, R = \frac{Z_0}{\alpha\ell}, L = \frac{1}{\omega_0^2 C}$$
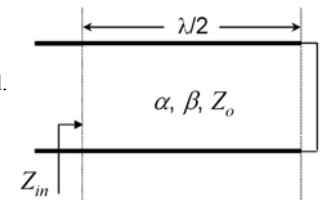
$$Q = \omega_0 RC = \frac{\beta}{2\alpha}, \ell = \frac{\pi}{\beta} \text{ at resonance.}$$



Equivalent circuit :

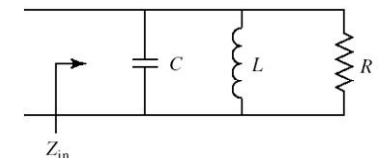

12

Example 6.2

A half-wave microstrip resonator

50-Ω line, $\lambda/2$ resonator, $d = 1.59$ mm, $\epsilon_r = 2.2$, $\tan \delta = 10^{-3}$, $f = 5$ GHz.

Calculate its Q value.

Sol: $Z_0 = 50 \Omega$, $d = 1.59$ mm, and $\epsilon_r = 2.2 \Rightarrow W = 4.9$ mm, $\epsilon_{\text{reff}} = 1.87$.


$$\ell = \lambda/2 = c / (2f \sqrt{\epsilon_{\text{reff}}}) = 21.9 \text{ mm}$$

$$\beta = 2\pi/\lambda = 143.2 \text{ rad/m}$$

$$\alpha_c = R/Z_0 W = 0.075 \text{ Np/m}$$

$$\alpha_d = \dots = 0.0611 \text{ Np/m}$$
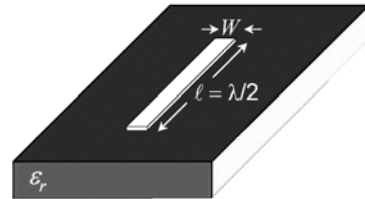
$$Q = \beta/2\alpha = \beta/2(\alpha_c + \alpha_d) = 526.$$



13

6.3 Rectangular Waveguide Cavity

TE_{mn}, TM_{mn} modes :

$$E_t(x, y, z) = \underline{e}(x, y) \left(A^+ e^{-j\beta_{mn}z} + A^- e^{+j\beta_{mn}z} \right)$$


$$\beta_{mn} = \sqrt{k^2 - \left(\frac{m\pi}{a} \right)^2 - \left(\frac{n\pi}{b} \right)^2}$$

For a resonant cavity, $\underline{E}_t = 0$, at $z = 0, d$

$$\beta_{mn}d = \ell\pi, \ell = 1, 2, 3, \dots$$

$$k_{mn\ell} = \sqrt{\left(\frac{m\pi}{a} \right)^2 + \left(\frac{n\pi}{b} \right)^2 + \left(\frac{\ell\pi}{d} \right)^2}$$
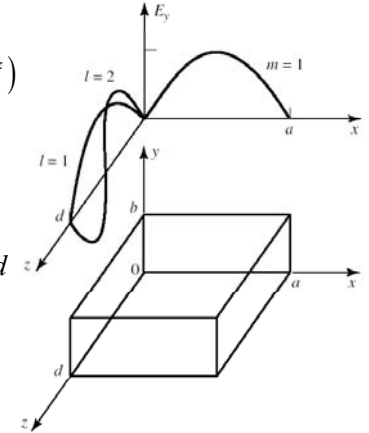
$$f_{mn\ell} = \frac{c}{2\pi} \frac{k_{mn\ell}}{\sqrt{\mu_r \epsilon_r}}$$



14

Q-Factor of a TE_{10l} Cavity

➤ Total fields:

$$E_y = E_0 \sin \frac{\pi x}{a} \sin \frac{\ell \pi z}{d}$$

$$H_x = -j \frac{E_0}{Z_{TE}} \sin \frac{\pi x}{a} \cos \frac{\ell \pi z}{d}$$

$$H_z = -j \frac{j\pi E_0}{ka\eta} \cos \frac{\pi x}{a} \sin \frac{\ell \pi z}{d}$$

➤ Q factor $\Rightarrow W_e, P_c$, and P_d

$$W_e = \frac{\epsilon}{4} \iiint |\underline{E}|^2 dv = \frac{abd}{16} \epsilon E_0^2$$


$$W_m = \frac{\epsilon}{4} \iiint |\underline{H}|^2 dv = \frac{abd}{16} \mu E_0^2 \left(\frac{1}{Z_{TE}^2} + \frac{\pi^2}{k^2 a^2 \eta^2} \right) = W_e$$

$$P_c = \frac{1}{2} \iint_{\text{walls}} |H_t|^2 ds = \frac{R_s E_0^2 \lambda^2}{8\eta^2} \left(\frac{\ell^2 ab}{d^2} + \frac{bd}{a^2} + \frac{\ell^2 a}{2d} + \frac{d}{2a} \right)$$

$$Q_c = \omega_0 \frac{2W_e}{P_c} = \frac{(kad)^3 b\eta}{2\pi^2 R_s} \frac{1}{2\ell^2 a^3 b + 2bd^3 + \ell^2 a^3 d + ad^3}$$

$$P_d = \frac{\omega \epsilon''}{2} \iiint |\underline{E}|^2 dv = \frac{\omega \epsilon''}{2} \frac{abd}{4} E_0^2$$
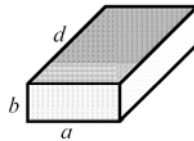
$$Q_d = \omega_0 \frac{2W_e}{P_d} = \frac{\epsilon'}{\epsilon''} = (\tan \delta)^{-1}$$



15

Example 6.3

Design of a Rectangular Waveguide Cavity

$a = 40$ mm, $b = 20.0$ mm, $\epsilon_r = 2.25$, $\tan \delta = 4 \times 10^{-4}$. If $f = 5$ GHz, find d and Q values for $\ell = 1$.

Sol:

$$k = \frac{\omega}{c} \sqrt{\epsilon_r} = \frac{2\pi \times 5 \times 10^9}{3 \times 10^{10}} \sqrt{2.25} = 1.5708 \text{ cm}^{-1}$$

$$\beta d = \ell\pi \Rightarrow d = \frac{\ell\pi}{\sqrt{k^2 - \left(\frac{\pi}{a} \right)^2}} = \mathbf{23.05} \text{ mm, for } \ell = 1.$$

$$R_s = 1.84 \times 10^{-2} \Omega (\text{copper@5GHz}), \eta = \frac{120\pi}{\sqrt{\epsilon_r}} = 251.3 \Omega$$


$$Q_d = (\tan \delta)^{-1} = 2500, Q_c = \mathbf{8370}, \ell = 1.$$

$$Q = \left(\frac{1}{Q_c} + \frac{1}{Q_d} \right)^{-1} = \left(\frac{1}{8370} + \frac{1}{2500} \right)^{-1} = \mathbf{1925}, \ell = 1.$$


16

6.6 Excitation of Resonators

Gap-Coupling to a
Micro resonator cavity

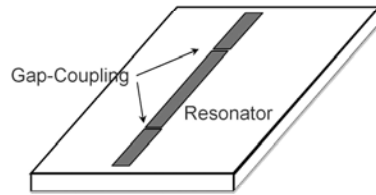

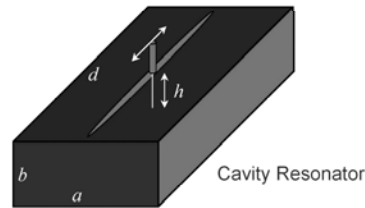
Probe-coupling to
A rectangular WG cavity



- (1) The penetration depth h is tunable
For impedance adjustment.
- (2) The probe can be sliding along z .

17


Coupling to Microwave Resonators

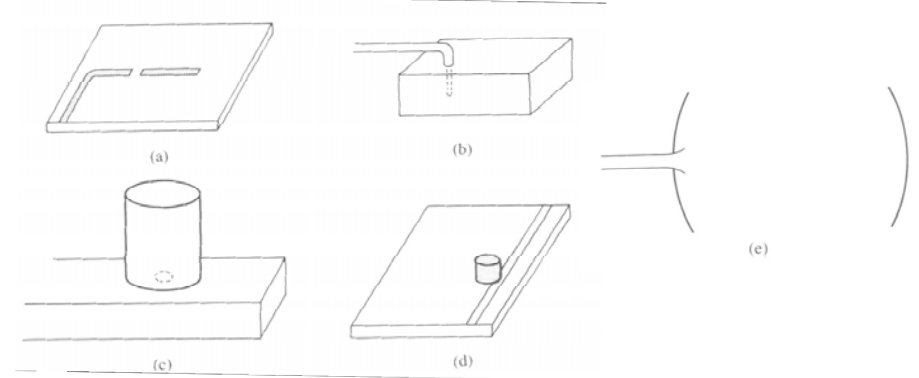

- (a) A microstrip transmission line resonator gap coupled to a microstrip feed line.
- (b) A rectangular cavity resonator fed by a coaxial probe.
- (c) A circular cavity resonator aperture coupled to a rectangular waveguide.
- (d) A dielectric resonator coupled to a microstrip feed line.
- (e) A Fabry-Perot resonator fed by a waveguide horn antenna.

18

A Gap-Coupled Microstrip Resonator

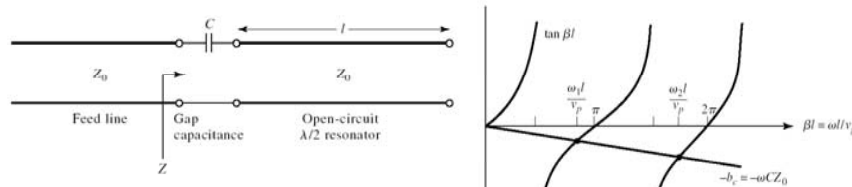

- Temporarily treat the lossy resonator as losses and apply the concept of *complex frequency* to evaluate its loss term R

$$b_c = Z_0 \omega C; \quad z_{in} = \frac{Z_{in}}{Z_0} = -j \frac{\frac{1}{\omega C} + Z_0 \cot \beta \ell}{Z_0} = -j \frac{b_c + \tan \beta \ell}{b_c \tan \beta \ell}$$

- Resonance occurs at $z_{in} = 0$, $b_c + \tan \beta \ell = 0$, $\tan \beta \ell = -b_c$,
- If $b_c \ll 1$, ω_1 is close to the first resonant frequency of the unloaded resonator.
- The coupling of the capacitor C will lower its resonant frequency.

19

The Coupling Coefficient g

$$b_c = Z_0 \omega C$$

$$z_{in} = \frac{Z_{in}}{Z_0} = -j \frac{\frac{1}{\omega C} + Z_0 \cot \beta \ell}{Z_0}$$

$$= -j \frac{b_c + \tan \beta \ell}{b_c \tan \beta \ell}$$

$$\frac{dz_{in}(\omega)}{d\omega} = -j \frac{\sec^2 \beta \ell}{b_c \tan \beta \ell} \frac{d(\beta \ell)}{d\omega} = j \frac{(1+b_c^2)}{b_c^2} \frac{\ell}{v_p} \approx j \frac{1}{b_c^2} \frac{\ell}{v_p} = j \frac{\pi}{\omega_1 b_c^2}$$

$$z_{in}(\omega) = z_{in}(\omega_1) + (\omega - \omega_1) \frac{dz_{in}(\omega)}{d\omega} \bigg|_{\omega_1} + \dots = (\omega - \omega_1) \frac{j\pi}{\omega_1 b_c^2} \frac{\omega_1 \left(1 + \frac{1}{2Q}\right)}{\omega_1 b_c^2} \rightarrow \frac{\pi}{2Q b_c^2} + \frac{j\pi(\omega - \omega_1)}{\omega_1 b_c^2}$$

The input resistance $R = \frac{Z_0 \pi}{2Q b_c^2}$ and coupling coefficient $g = \frac{Z_0}{R} = \frac{2Q b_c^2}{\pi}$.


$b_c < \sqrt{\pi/2Q}$, $g < 1$, undercoupled

$b_c = \sqrt{\pi/2Q}$, $g = 1$, critically coupled

$b_c > \sqrt{\pi/2Q}$, $g > 1$, overcoupled

20

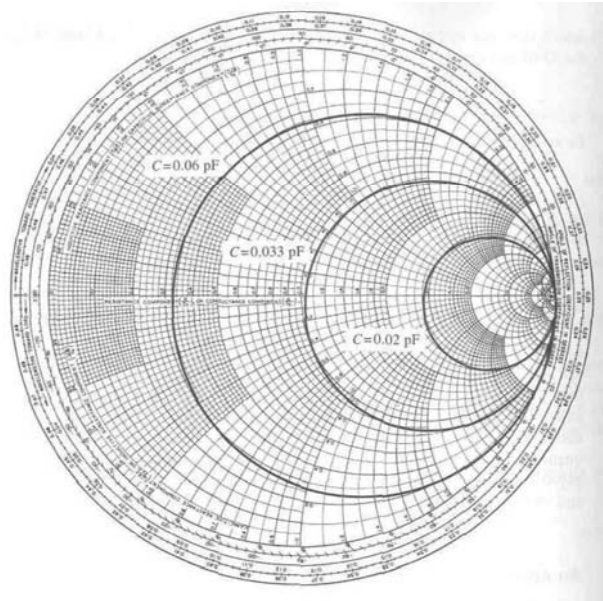Smith chart for the gap-coupled microstrip resonator



21

Example 6.6

Design of Gap-Coupled Microstrip Resonator

50-Ω microstrip feedline, 50-Ω microstrip $\lambda/2$ resonator with $\ell = 21.75$ mm, $\epsilon_{\text{reff}} = 1.9$, $\alpha = 0.001$ dB/mm. Find the coupling capacitor and the resonant frequency f_1 .

Sol:

$$f_0 = \frac{v_p}{\lambda_g} = \frac{c}{2\ell\sqrt{\epsilon_{\text{reff}}}} = \frac{3 \times 10^{11}}{2 \times 21.75 \times \sqrt{1.9}} = 5 \text{ GHz}$$

$$Q = \frac{\beta}{2\alpha} = \frac{\pi}{2\ell\alpha} = 628 (\text{or } 200 \times \pi)$$

$$b_c = \sqrt{\frac{\pi}{2Q}} = \sqrt{\frac{\pi}{2 \times 200\pi}} = 0.05$$


$$C = \frac{b_c}{\omega Z_0} = \frac{0.05}{2\pi \times 5 \times 10^9 \times 50} = 0.032 \text{ pF}$$

$$f_1 = 4.918 \text{ GHz (obtained by a root-searching process)}$$

22

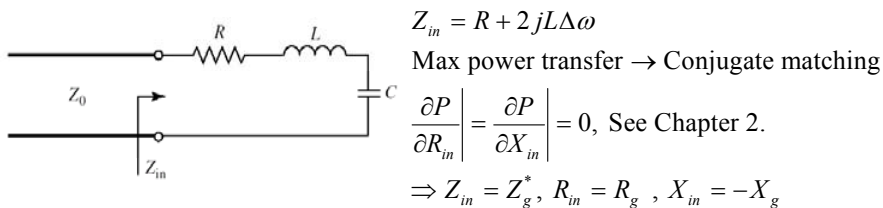6.6 Excitation of Resonators


Critical coupling : A resonator is matched to a feedline to have *max power* transfer at resonant frequency.



- At resonance, $\omega = \omega_0$, or $\Delta\omega = 0$, $Z_{in} = R = Z_0$
 Unloaded $Q = \omega_0 L / R$
 External $Q_e = \omega_0 L / Z_0$
- Coupling coefficient $g = Q / Q_e = Z_0 / R$
 $g < 1$, resonator is undercoupled to the feedline.
 $g = 1$, resonator is critically coupled to the feedline.
 $g > 1$, resonator is overcoupled to the feedline.

23

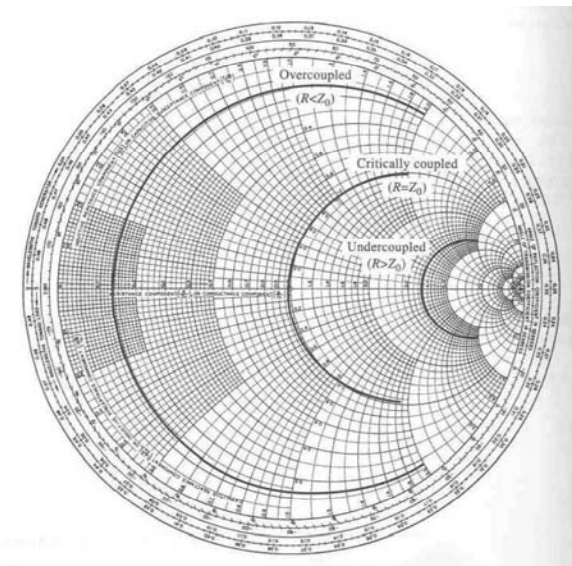Smith chart illustrating coupling to series RLC circuit



24